

How Do Electrical Circuits Work?
(Chapter 3 Lesson 2)

1. Explain what circuit in series is: _____

Draw and label a series circuit:

2. Define a parallel circuit:

Draw and Label a parallel circuit

3. What is the difference between an open and a closed circuit?

4. Discuss three ways that you can use electricity safely.
